

لصفحة

ع.ع.



**FACULTY OF ELECTRONIC ENGINEERING, MENOUF  
ELECTRONIC AND ELECTRICAL COMMUNICATIONS DEPARTMENT**

**SUBJECT: NETWORK THEORY, 3<sup>rd</sup> YEAR**      **TIME ALLOWED: THREE HOURS**

**DATE OF EXAMINATION: Sunday, 29/12/2019**      **TOTAL MARKS: 70 MARKS**

**ANSWER THE FOLLOWING QUESTIONS**

1. Find the two Foster realizations of the driving point impedance  $Z(s)$  if

$$|Z(j\omega)|^2 = (\omega^4 + 45\omega^2 + 324) / (\omega^4 + 17\omega^2 + 16) \quad (14 \text{ Marks})$$

2. Synthesize the transfer function  $H(s) = V_2(s) / V_1(s)$  of a singly  $1-\Omega$  terminated FTN using the two port parameters if

$$|H(j\omega)|^2 = \omega^6 / (\omega^6 + 1) \quad (8 \text{ Marks})$$

3.a: From the first principles determine the element values required for a symmetrical T-section LPF, suitable for insertion in a  $600 \Omega$ , if the attenuation,  $\alpha$ , at a frequency  $f = 2 \text{ MHz}$ , is  $22.87819259 \text{ dB}$ .

3.b: Using the results obtained in (3.a), determine the magnitude of  $Z_{cT}$  at  $f = 2f_c$  and the phase shift,  $\beta$ , at  $f = f_c$ .      (8 Marks)

4. If the transfer function is  $H(s) = V_2(s) / I_1(s)$ , the impedance level is  $10^3 \Omega$  and the amplitude function of the Butterworth filter is  $|H(j\omega)|^2 = 1 / (1 + \omega^{2n})$ ;  $n = 1, 2, 3$ , design a 3<sup>rd</sup> order Butterworth to stop all radiant frequencies between  $10^4 \text{ rad/sec}$ . and  $4 \times 10^4 \text{ rad/sec}$ .      (20 Marks)

5. If the transfer function is  $H(s) = V_2(s) / V_1(s)$ ,  $\omega_c = 10^4 \text{ rad/sec}$ ,  $R_o = 1 \Omega$  and the ripple in the pass-band must not exceed  $0.5 \text{ dB}$ , synthesize a 3<sup>rd</sup> order Chebyshev high-pass filter.      (20 Marks)

**GOOD LUCK**

المحرر  
2019/12/29  
Dr. Mohamed El-Halawany